SOC Design

Lab-3 FIR

110590022 陳冠晰

Function specification

•
$$y[t] = \Sigma (h[i] * x[t - i])$$

In signal processing, a finite-impulse-response, or finite impulse response models are generally linear dynamic models characterized by finite-order moving average representations, implying that their responses to impulse inputs go to zero after a finite number of time steps, equal to the model's memory length.


FIR filters can be discrete-time or continuous-time, and digital or analog.

$$egin{align} y[n] &= b_0 x[n] + b_1 x[n-1] + \dots + b_N x[n-N] \ &= \sum_{i=0}^N b_i \cdot x[n-i], \end{split}$$


Where:

- x[n] is the input signal,
- . y[n] is the output signal,
- . N is the filter order; an N_{th} -order filter has N+1 terms on the right-hand side
- . b_i is the value of the impulse response at the ith instant for $0 \le I \le N$ of an Nth-order FIR filter. If the filter is a direct form FIR filter, then b_i is also a coefficient of the filter.

Block Diagram

 

Tap_RAM / Data_RAM

 

Tape RAM:

8,610000000

Tape address: 0x80 - 0xFF

EN = (AW[3]:8]==0)|(AR[3]:8]==0)&(AW[1]|AR[1])

Check if read/write address belongs to TapeRAM

WE = (AWvalid & & Wvalid == 1)? 4'b1111: 4'b0000; Check if address/data write is valid

A = AW[5:0] AW will >72, 4-bit left, still can represent the address of 11 tapes

Di = Wdata Data-in equals to wdata of AXI-Lite (hti] flow through TogetAM by avilite)

Awready = 1 (中M 尚有空間)

wready = 1 (Puta Proffer 前有 space)

Data RAM:

EN = 55_tvalid (55_tlast = 0)


WE = (55_tready & 55_idle)? 4'b 1111: 4'b 0000; (Ready to write New volue" & not finish)

A = (ap_ctrl [2] && init_addr < 6'd44)? init_addr: data_A_tmp;

If ap_idle == 1, initialize the value in dataRAM.


Pi = 55_tdata

 FSM for ap_ctrl: (apstart, ap_done, ap_idle)



- 1. 左上角的 FSM 是用來給 ap_start, ap_done, ap_idle 的,一開始處在 INIT state,ap_ctrl = {ap_idle, ap_done, ap_start} = 3'b100,當我們 Host 端 (testbench) program ap_start,代表 FIR 開始運作,ap_idle 降下,進到 IDLE state,ap_ctrl = {ap_idle, ap_done, ap_start} = 3'b000。當我們完成最後一個 Y 的計算,傳出去給 testbench 比對,同時拉高 sm_tlast,就代表 FIR 做完運算,進到 DONE state,ap_ctrl = {ap_idle, ap_done, ap_start} = 3'b010。由於 testbench 需要讀取 ap_done 的訊號,所以要等到 read address == 0x00 讀取到 ap_done 過後再回到 initial 的 state。
- 2. 左下角的 FSM 專門產生 ss_idle 的訊號拿去 data_RAM 當成 write enable,在 還未收到 ss_tlast 的期間,都會是 1,等到收到 ss_tlast,才會進到 SS_DONE state, ss_idle = 0,代表不能再寫了。
- 3. 右邊的 FSM 是在產生 sm_tlast,當最後一個 Y 計算完,counter 數到 data length,就進到 SM DONE state, sm tlast 拉高一個 cycle。

Operation

 

sm_tvalid 拉高,代表計算出的 Y 被拿去 testbench 做比對。 上圖最下面是做完 operation pipeline 後呈現出的 timing waveform,可以看到中間圖片中,X stream-in 和 Y stream-out 間變化。


Resource usage


Slice LUTs* 190 0 0 53200 0.36 LUT as Logic 190 0 0 53200 0.36 LUT as Memory 0 0 0 17400 0.00 Slice Registers 224 0 0 106400 0.21 Register as Flip Flop 224 0 0 106400 0.21 Register as Latch 0 0 0 106400 0.00 F7 Muxes 0 0 0 13300 0.00 13300 0.00 13300 0.00 13300 0.00 13300 0.00 13300 0.00 13300 0.00 13300 0.00 13300 0.00 13300 0.00 13300 0.00 13300 0.00 13300 0.00 13300 0.00 13300 0.00 13300 0.00 13300 0.00 0.00 13300 0.00 0	Site Type	Used	Fixed	Prohibited	Available	++ Util%
Fo makes	LUT as Logic LUT as Memory Slice Registers Register as Flip Flop Register as Latch	190 0 224 224 0	0 0 0 0	0 0 0	53200 17400 106400 106400 106400	0.36 0.00 0.21 0.21 0.00

Site Type	U	sed		Fixed	Prohibited	
Block RAM Tile RAMB36/FIFO* RAMB18	 	0 0 0	 	0 0 0	0 0 0	140 0.00 140 0.00

Timing report




 

 


Simulation waveforms


Coefficient

 

X-in / Y-out

 

RAM access control

 

可以看到一開始 tap Di 在 load in coefficients,再來是 data 的 stream in。